

Apresentação

Trabalho 2 - Sistemas Digitais

2018/2

Neander em VHDL

Nome: Gabriel Martins dos Santos

Cartão : 00275617

Introdução

Este trabalho tem como objetivo implementar as instruções do processador NEANDER, e seus respectivos componentes e máquina de estados, através da linguagem de descrição VHDL.

Além das 11 instruções primárias do neander foram adicionadas as instruções de subtração e multiplicação.

Ao longo do trabalho foram adicionados três programas utilizando as instruções do NEANDER, os programas 1 e 2 utilizam as instruções primárias, o programa 3 usa as instruções adicionais desenvolvidas para o projeto:

1. Somador de matrizes de 4 bits 2×2 .
2. Multiplicador de matrizes de 4 bits 2×2 .
3. Subtração de endereços de memória.

Definições

Características do NEANDER:

- Largura dos endereços e dados de 8 bits
- Dados representados em complemento de dois
- 1 acumulador de 1 byte (AC)
- 1 apontador de programa de 1 byte (PC)
- 1 registrador de estado que indica dados negativos ou zero
- Modo de endereçamento direto

Definições

11 Instruções primárias :

Código	Instrução	Comentário
0000	NOP	nenhuma operação
0001	STA end	armazena acumulador - (store)
0010	LDA end	carrega acumulador - (load)
0011	ADD end	soma
0100	OR end	“ou” lógico
0101	AND end	“e” lógico
0110	NOT	inverte (complementa) acumulador
1000	JMP end	desvio incondicional - (jump)
1001	JN end	desvio condicional - (jump on negative)
1010	JZ end	desvio condicional - (jump on zero)
1111	HLT	término de execução - (halt)


2 Instruções Implementadas:

1011 - SUB end


1100 - MULT end

Definições


Instruções com um byte: NOP, NOT, HLT

 

 Instruções com dois bytes: STA, LDA, ADD, OR, AND, JMP, JN, JZ





Definições

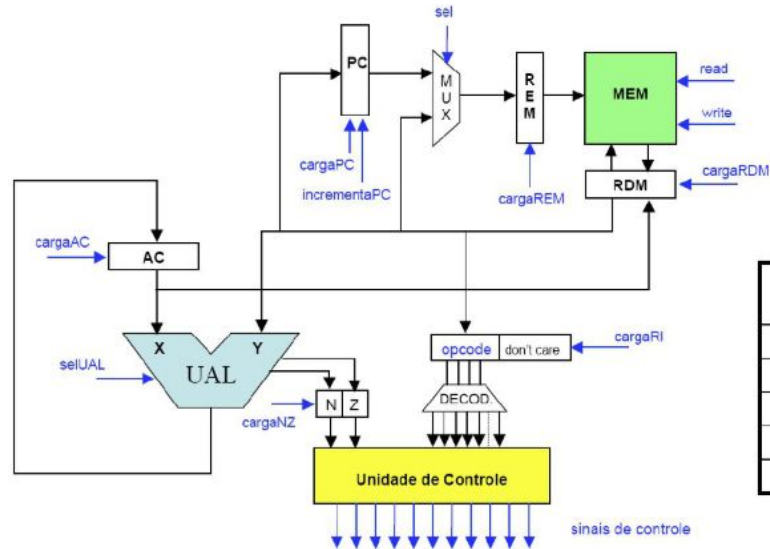

operações da UAL	selUAL
X + Y	000
X and Y	001
X or Y	010
Not X	011
Y	100

RTL do circuito

 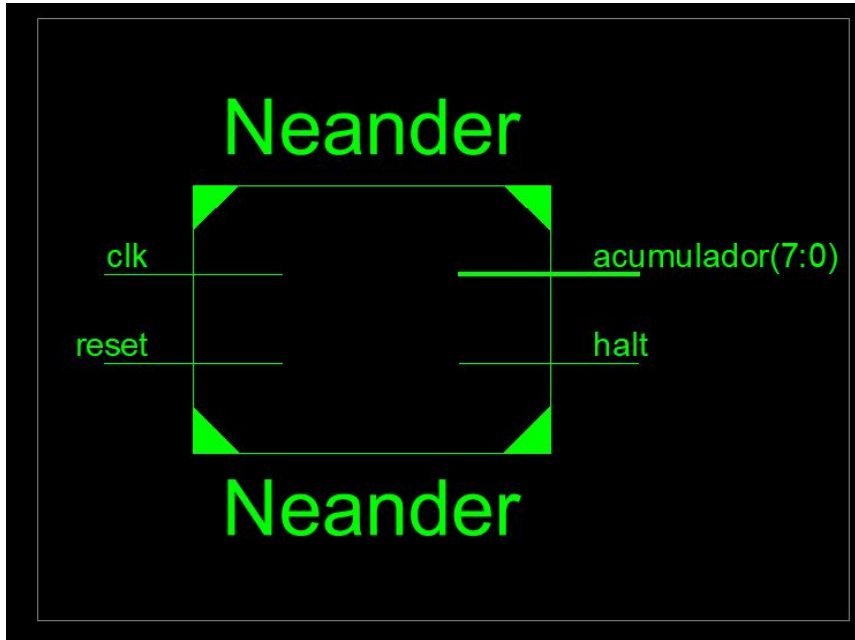

Tempo

Timing Summary:

Speed Grade: -5

Minimum period: 10.707ns (Maximum Frequency: 93.393MHz)
Minimum input arrival time before clock: 3.788ns
Maximum output required time after clock: 7.612ns
Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

=====

Timing constraint: Default period analysis for Clock 'clk'
Clock period: 10.707ns (frequency: 93.393MHz)
Total number of paths / destination ports: 11346 / 186

Delay: 10.707ns (Levels of Logic = 14)
Source: Instancia_7/entrada_7 (FF)
Destination: Instancia_9/dado_0 (FF)
Source Clock: clk rising
Destination Clock: clk rising

Resultados Obtidos


Dados da Unidade de Controle e ULA:

```
Synthesizing Unit <ULA>.
Related source file is "C:/Neander_Gabriel_Martins/ULA.vhd".
Found 8x8-bit multiplier for signal <mult>.
Found 8-bit addsub for signal <operacao$addsub0000>.
Summary:
    inferred    1 Adder/Subtractor(s).
    inferred    1 Multiplier(s).
Unit <ULA> synthesized.

Synthesizing Unit <UnidadeControle>.
Related source file is "C:/Neander_Gabriel_Martins/UnidadeControle.vhd".
Found finite state machine <FSM_0> for signal <state>.
-----
| States          | 9 |
| Transitions    | 48 |
| Inputs         | 12 |
| Outputs        | 9 |
| Clock          | clkDiv (rising_edge) |
| Reset          | reset (positive) |
| Reset type     | asynchronous |
| Reset State    | s0 |
| Power Up State | s0 |
| Encoding       | automatic |
| Implementation | LUT |
-----
Found 1-bit register for signal <clkDiv>.
Found 32-bit up counter for signal <cont>.
Summary:
    inferred    1 Finite State Machine(s).
    inferred    1 Counter(s).
    inferred    1 D-type flip-flop(s).
Unit <UnidadeControle> synthesized.
```

Número de FF's , LUT4 Utilizados

Neander Project Status (10/17/2018 - 19:25:05)			
Project File:	Neander_Gabriel_Martins.xise	Parser Errors:	No Errors
Module Name:	Neander	Implementation State:	Placed and Routed
Target Device:	xc3s100e-5cp132	• Errors:	No Errors
Product Version:	ISE 14.7	• Warnings:	66 Warnings (1 new)
Design Goal:	Balanced	• Routing Results:	All Signals Completely Routed
Design Strategy:	Xilinx Default (unlocked)	• Timing Constraints:	All Constraints Met
Environment:	System Settings	• Final Timing Score:	0 (Timing Report)

 Device Utilization Summary					
Logic Utilization	Used	Available	Utilization	Note(s)	
Number of Slice Flip Flops	85	1,920	4%		
Number of 4 input LUTs	157	1,920	8%		
Number of occupied Slices	121	960	12%		
Number of Slices containing only related logic	121	121	100%		
Number of Slices containing unrelated logic	0	121	0%		
Total Number of 4 input LUTs	203	1,920	10%		
Number used as logic	157				
Number used as a route-thru	46				
Number of bonded IOBs	11	83	13%		
Number of RAMB16s	1	4	25%		
Number of BUFGMUXs	1	24	4%		
Number of MULT18X18SIOs	1	4	25%		
Average Fanout of Non-Clock Nets	3.46				

Memória utilizada / Erros / 4LUTs detalhados

```
Target Device : xc3s100e
Target Package : cpl32
Target Speed : -5
Mapper Version : spartan3e -- $Revision: 1.55 $
Mapped Date : Wed Oct 17 19:24:32 2018

Design Summary
-----
Number of errors:      0
Number of warnings:   56
Logic Utilization:
  Number of Slice Flip Flops:      85 out of 1,920  4%
  Number of 4 input LUTs:         157 out of 1,920  8%
Logic Distribution:
  Number of occupied Slices:       121 out of 960  12%
  Number of Slices containing only related logic: 121 out of 121 100%
  Number of Slices containing unrelated logic:    0 out of 121  0%
  *See NOTES below for an explanation of the effects of unrelated logic.
Total Number of 4 input LUTs:     203 out of 1,920  10%
  Number used as logic:            157
  Number used as a route-thru:     46

The Slice Logic Distribution report is not meaningful if the design is
over-mapped for a non-slice resource or if Placement fails.

Number of bonded IOBs:            11 out of 83  13%
Number of RAMB16s:                 1 out of 4  25%
Number of BUFMUXs:                 1 out of 24  4%
Number of MULT18X18SIOs:           1 out of 4  25%

Average Fanout of Non-Clock Nets: 3.46

Peak Memory Usage: 4432 MB
Total REAL time to MAP completion: 2 secs
Total CPU time to MAP completion: 1 secs
```


Delay

Generating "PAR" statistics.

Generating Clock Report

Clock Net	Resource	Locked	Fanout	Net Skew(ns)	Max Delay(ns)
clk_BUFGP	BUFGMUX_X2Y10	No	60	0.024	0.057
Instancia_11/clkDiv	Local		4	0.009	1.287

Simulações - ULA

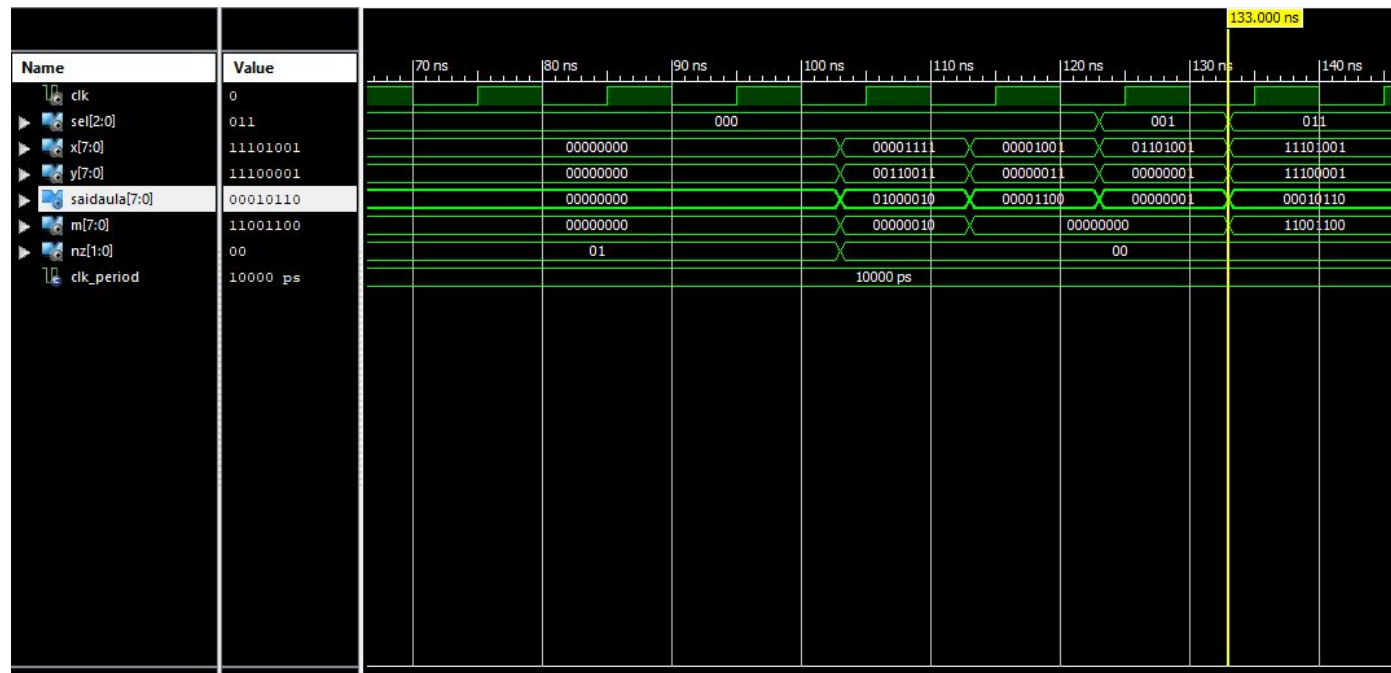


operações da UAL	selUAL
X + Y	000
X and Y	001
X or Y	010
Not X	011
Y	100

Simulações - ULA




operações da UAL	selUAL
X + Y	000
X and Y	001
X or Y	010
Not X	011
Y	100

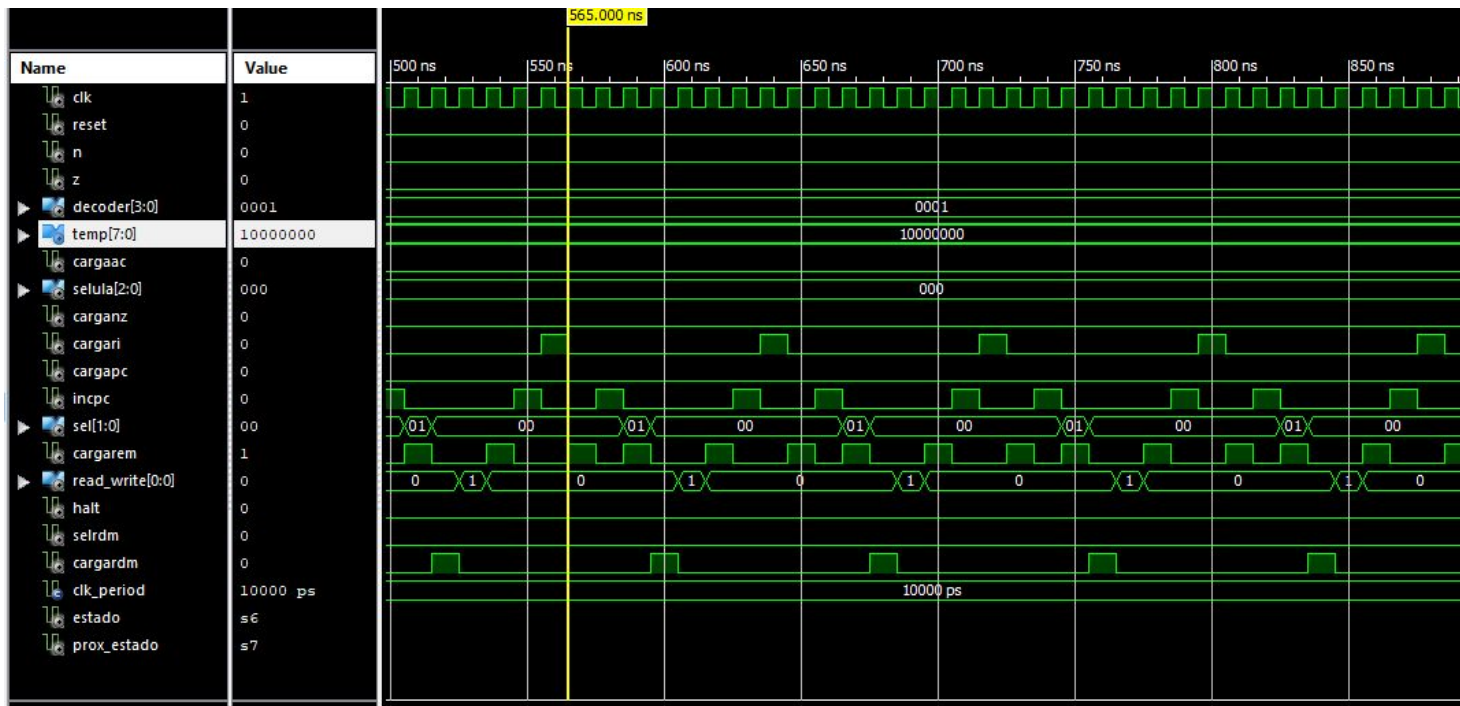Simulações: Unidade Controle - Teste com LDA



Simulações: Neander Completo

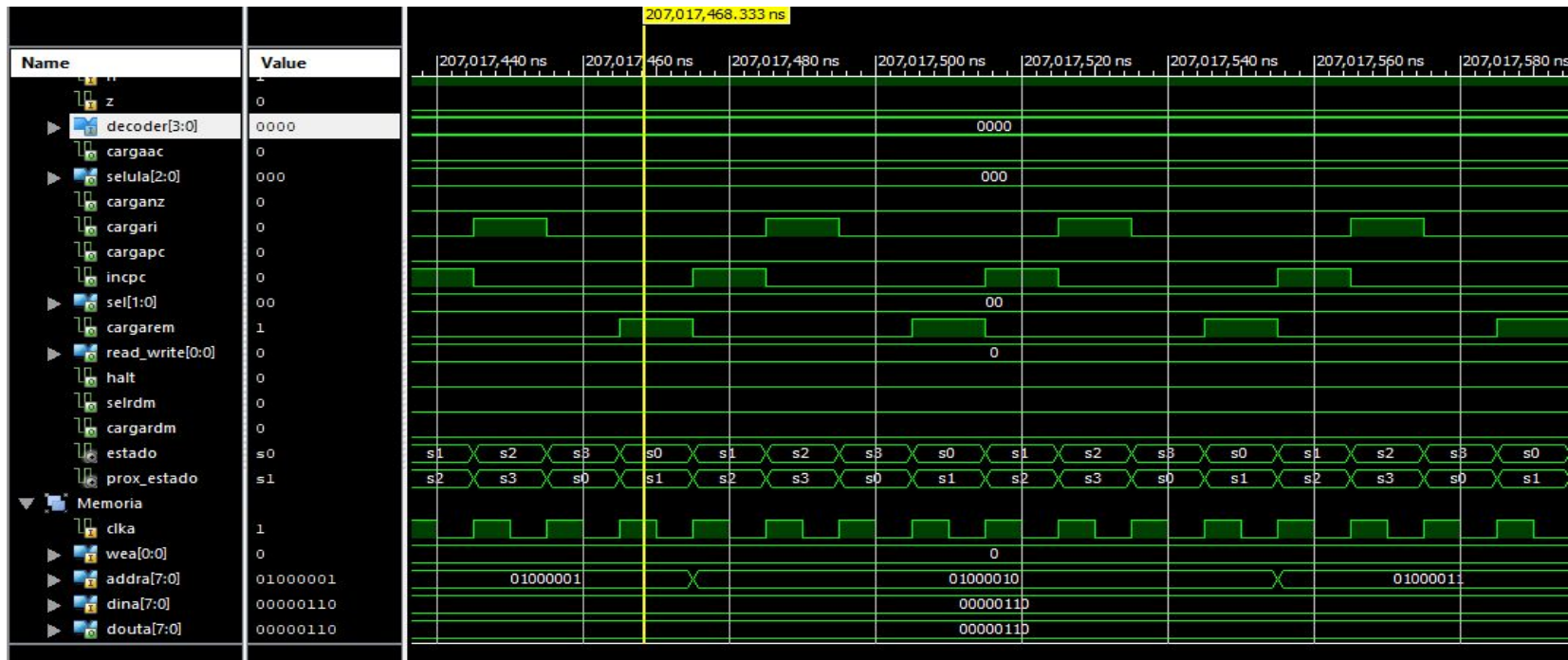

Prog 1 - Soma de Matrizes

Resultado

$$A + B = \begin{bmatrix} 2,00 & 4,00 \\ 6,00 & 8,00 \end{bmatrix}_{(2 \times 2)}$$

Matriz A

$$A = \begin{bmatrix} 1,00 & 2,00 \\ 3,00 & 4,00 \end{bmatrix}_{(2 \times 2)}$$

Matriz B

$$B = \begin{bmatrix} 1,00 & 2,00 \\ 3,00 & 4,00 \end{bmatrix}_{(2 \times 2)}$$

Prog 1 - Soma de Matrizes

NOP
 LDA 30
 ADD 34
 STA 38
 LDA 31
 ADD 35
 STA 39
 LDA 32
 ADD 36
 STA 40
 LDA 33
 ADD 37
 STA 41
 HLT


0	0	32	30	48	34	16	38	32	31	48	35	16	39	32	32
16	36	16	40	32	33	48	37	16	41	240	0	0	0	0	1
32	3	4	1	2	3	4	2	4	6	8	0	0	0	0	0
48	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
64	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
80	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
96	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
112	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
128	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
144	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
160	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
176	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
192	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
208	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
224	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
240	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

13 instruções

235 ciclos de relógio

4700 ns (operando a 50MHz)

Prog 1 - Soma de Matrizes - Simulação c/ atraso

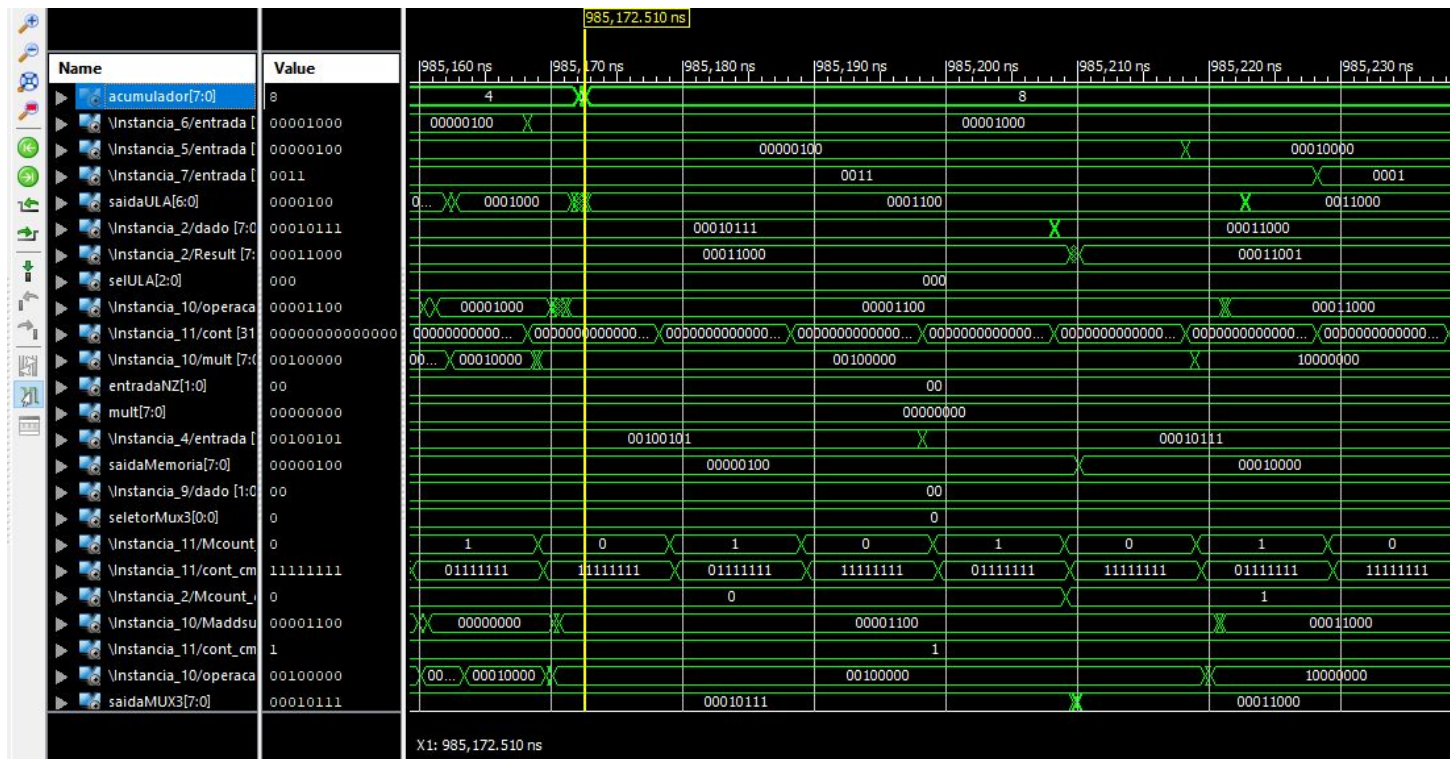

Prog 2 - Multiplicação de Matrizes

Resultado

$$Ax B = \begin{bmatrix} 7,00 & 10,00 \\ 15,00 & 22,00 \end{bmatrix}_{(2 \times 2)}$$

Matriz A

$$A = \begin{bmatrix} 1,00 & 2,00 \\ 3,00 & 4,00 \end{bmatrix}_{(2 \times 2)}$$

Matriz B

$$B = \begin{bmatrix} 1,00 & 2,00 \\ 3,00 & 4,00 \end{bmatrix}_{(2 \times 2)}$$

Prog 2 - Multiplicação de Matrizes


```

NOP
LDA 80
MUL 84
STA 88
LDA 82
MUL 85
STA 89
LDA 80
MUL 86
STA 90
LDA 82
MUL 87
STA 91
LDA 81
MUL 84
STA 92
LDA 83
MUL 85
STA 93
LDA 81
MUL 86
STA 94
LDA 83
MUL 87
STA 95
LDA 88
ADD 89
STA 96
LDA 90
ADD 91
STA 97
LDA 92
ADD 93
STA 98
LDA 94
ADD 95
STA 99
HLT
    
```

	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	32	80	192	84	16	88	22	82	192	85	16	89	32	80	192
16	86	16	90	32	82	192	87	16	91	32	81	192	84	16	92	32
32	22	192	85	16	93	32	81	192	86	16	94	32	83	192	87	16
48	95	32	88	48	89	16	96	32	90	48	91	16	97	32	92	48
64	93	16	98	32	94	48	95	16	99	240	0	0	0	0	0	0
80	1	2	3	4	1	2	3	4	1	6	3	12	2	8	6	16
96	7	15	10	22	0	0	0	0	0	0	0	0	0	0	0	0
112	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
128	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
144	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
160	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
176	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
192	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
208	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
224	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
240	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

38 instruções
 605 ciclos de relógio
 12100 ns (operando a 50MHz)

Prog 2 - Multiplicação de Matrizes- Simulação c/ atraso

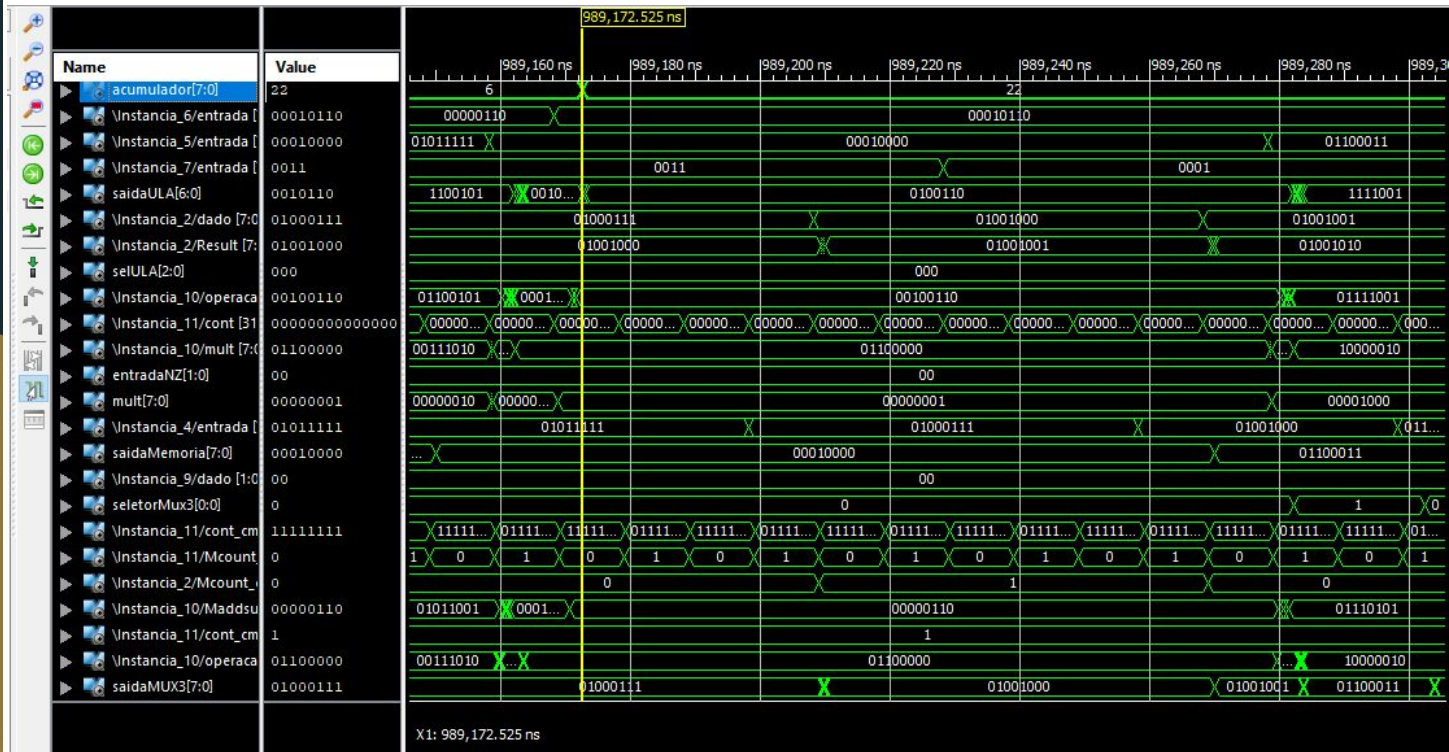

Prog 3 - Subtração de Endereços de Memória

NOP
LDA 17
SUB 18
STA 19
LDA 18
SUB 17
STA 20
HLT

	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	32	17	176	18	16	19	32	18	176	17	16	20	240	0	0
16	0	3	2	1	255	0	0	0	0	0	0	0	0	0	0	0
32	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
48	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
64	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
80	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
96	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
112	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
128	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
144	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
160	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
176	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
192	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
208	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
224	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
240	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

8 instruções
109 ciclos de relógio
2180 ns (operando a 50MHz)

Prog 3 - Subtração de Endereços de Memória- Simulação c/ atraso

